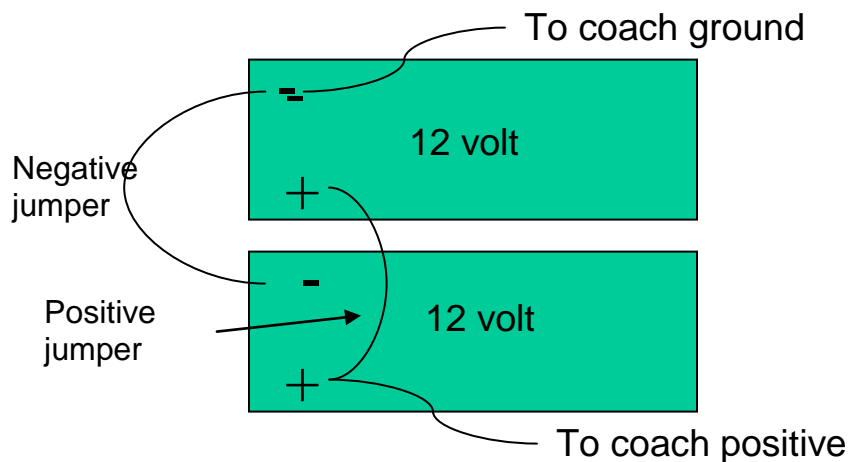


RVSurveysm


Replacing 12 volt coach batteries with 6 volt Golf Cart batteries

The process to replace the original 12 volt batteries with Golf Cart batteries is pretty simple, as long as you have the space for the batteries. Here is the original and converted wiring diagram:

12 Volt Battery Configuration



6 Volt Battery Configuration

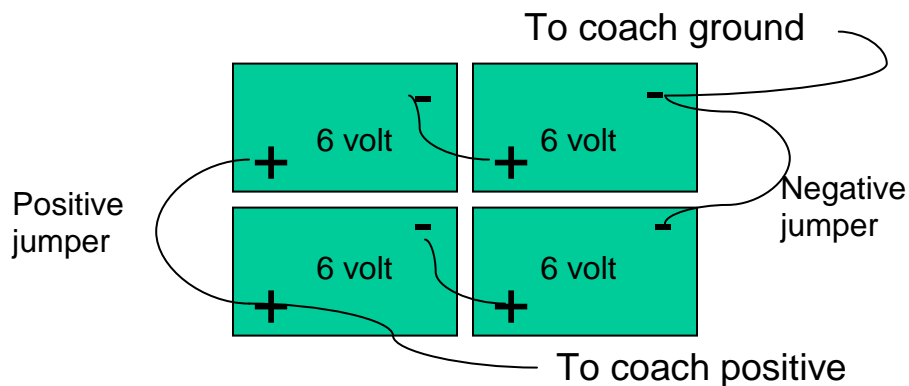

RVSurvey provides independent on-site RV inspections and a Do It Yourself RV Inspection Guide. See our web site for more information: <http://www.rvsurvey.com>